

[ESS12]

**UNIVERSITY OF BOLTON**

**SCHOOL OF ENGINEERING**

**BENG (HONS) ELECTRICAL AND ELECTRONIC  
ENGINEERING**

**SEMESTER TWO EXAMINATION 2018/2019**

**INTRODUCTORY DIGITAL ELECTRONICS**

**MODULE NO: EEE4013**

Date: Monday 20<sup>th</sup> May 2019

Time: 14:00 – 16:00

---

**INSTRUCTIONS TO CANDIDATES:**

There are SIX questions.

Answer ANY FOUR questions.

All questions carry equal marks.

Individual marks are shown within the question.

---

School of Engineering  
 BEng (Hons) Electrical and Electronic Engineering  
 Semester Two Examination 2018/2019  
 Introductory Digital Electronics  
 Module No. EEE4013

**Q1** a) What is the difference between the Gray code and Binary code?  
 Provide an example of where the Gray code can be used.

**[2 marks]**

b) Show how the binary code, 1100110, can be converted to its equivalent Gray code.

**[3 marks]**

c) Perform the following arithmetic operations. Please note carefully the radix (base) of the number system:

(i)  $2A_{16} + 6B_{16} = XX_{10}$

**[5 marks]**

(ii)  $1101_2 \times 1101_2 = XX_{10}$

**[5 marks]**

d) Complete the missing entries, **which are not shaded**, in the following figure Q1d. Please show all the steps that lead to the solution.

Hexadecimal	Binary	Decimal
	11010	?
	?	33
	?	105
A2	?	?


**Fig. Q1d**

**[10 marks]**

**Total 25 marks**

PLEASE TURN THE PAGE....

- Q2** a) For each circuit in figure Q2a below, determine if the LED should be on or off. Also provide the rationale behind your answer as well.

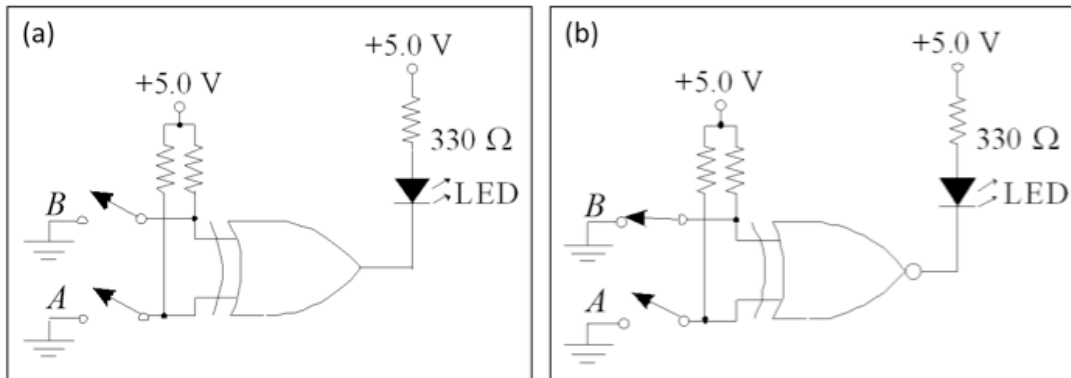

**Fig.Q2a: Digital circuits with LED**


[4 marks]

- b) Simplify the following Boolean expression using Boolean algebra and/or De Morgan's theorem.

$$X = \overline{\overline{A + AB} + C(A + \overline{AB})}$$

[5 marks]

- c) For the circuit shown in Fig. Q2c, construct a Truth Table for the logical functions at points C, D and Q. From the truth table obtained, identify a single logic gate that can be used to replace the complete circuit.

 

**Fig. Q2c: A two input digital circuit**

[6 marks]

Question 2 continues over the page....

PLEASE TURN THE PAGE....

Question 2 continued....

- d) Using a Karnaugh map, convert the following expressions to a minimised SOP (sum-of-product) form:

(i)  $X = \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C}D + A\bar{C}\bar{D} + A\bar{C}D + A\bar{B}C\bar{D}$

(ii)  $X = \bar{A}\bar{B} + A\bar{B}\bar{C} + A\bar{B}C + ABC$

[10 marks]

Total 25 marks

PLEASE TURN THE PAGE....


**Q3** a) For the circuit shown below (**Fig. Q3a**), the J-K inputs for both the flip-flops are tied to HIGH.

(i) With the help of appropriate waveforms, draw and describe the outputs from  $Q_A$  and  $Q_B$  ( $f_{out}$ ).

**[5 marks]**


(ii) If the input frequency ( $f_{in}$ ) has a clock frequency of 50 MHz what will be values of the frequencies available at  $Q_A$  and  $Q_B$ ?

**[5 marks]**

 

**Fig.Q3a: J-K flip flop circuit**

b) Determine the input conditions needed to produce  $x= 1$  for the circuit below (**Fig.Q3b**):

 

**Fig. Q3b: Digital circuit**

[5 marks]

Question 3 continues over the page....

PLEASE TURN THE PAGE....

Question 3 continued....

- c) Assuming the output of the decoder shown below (**Fig. Q3c**) is a logic "1". What are the inputs to the Active HIGH decoder and the logic expression of the decoder?


 


Fig. Q3c: a logic gate circuit

[5 marks]

- d) Determine the sum generated by the 8-bit parallel adder shown in **Fig.Q3d** below and show the intermediate carries when binary numbers  $A=10010110$  and  $B=10110011$  are added.

 


**Fig. Q3d: 8-bit parallel adder**

[5 marks]

**Total 25 marks**

**PLEASE TURN THE PAGE....**


- Q4** a) For an active HIGH input S-R latch being controlled by the S, R signals in the manner shown below (**Fig.Q4a**), draw the output signal showing the variation in the state of the output Q, assuming it is initially LOW.

 

**Fig. Q4a: Input wave form for a S-R latch**

[5 marks]

- b) It is often useful to be able to control the operation of a latch so that the inputs can be enabled (EN) at some times and disabled at others. Given a gated D-latch being controlled by the D and EN signals (**Fig.Q4b**), show the variation in the state of the output Q, assuming that Q is starting LOW.

 

**Fig. Q4b: Input wave form for a gated D-latch**

[5 marks]

School of Engineering  
BEng (Hons) Electrical and Electronic Engineering  
Semester Two Examination 2018/2019  
Introductory Digital Electronics  
Module No. EEE4013

- c) For a 1-bit half adder incorporating  $A$ ,  $B$  and  $C_{in}$  as the input signals and  $S$  and  $C_o$  as the output signals, you have been asked to reduce the number of logic gates in the circuit by utilizing multiplexers. Utilizing two 4:1 Mux, design a 1-bit full adder.

[10 marks]

Question 4 continues over the page....

PLEASE TURN THE PAGE....

Question 4 continued....

- d) For a negative-edge triggered J-K flip-flop being controlled by the following J, K signals (**Fig. Q4d**), show the variation of the output state Q, assuming Q is starting HIGH.

 


Fig.Q4d: Input waveform for J-K flip-flop


[5 marks]

Total 25 marks



PLEASE TURN THE PAGE....

- Q5** a) For the 5-bit register, show its states for the specified data input and CLK waveforms as shown in Fig. Q5a. Assume that the register is initially cleared.

 

**Fig. Q5a: 5 bit register**

**[7 marks]**

- b) For the BCD decade counter shown below (Fig. Q5b), assuming the J0 and K0 inputs are tied HIGH, draw the output waveforms for Q0, Q1, Q2 and Q3.

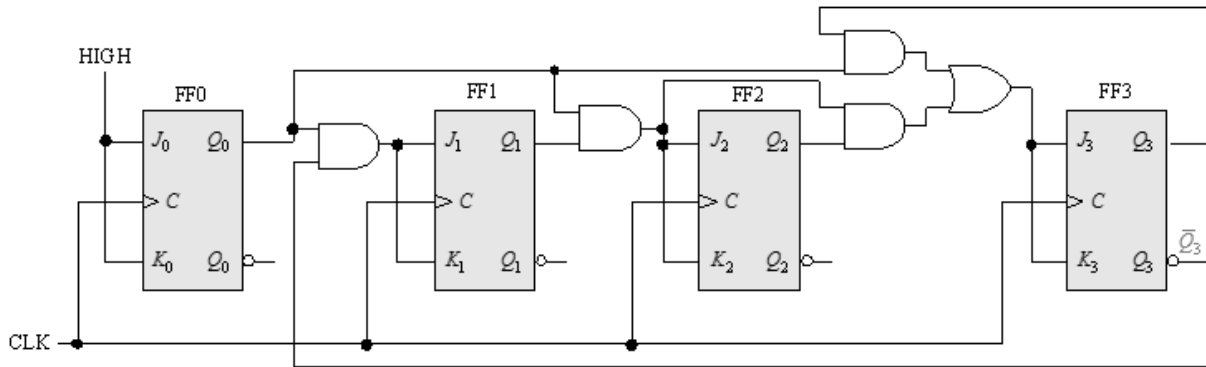


Fig. Q5b: BCD decade counter

[10 marks]

Question 5 continues over the page....

PLEASE TURN THE PAGE....

Question 5 continued....

- c) Using J-K flip-flops, design a 2-bit asynchronous counter and show its corresponding output waveforms.

[8 marks]

Total 25 marks

- Q6 a) Explain the difference between combinational and sequential circuits.

[2 marks]

- b) Explain the difference between latches and flip flops.

[2 marks]

- c) A circuit has four inputs and two outputs. The inputs, A3:0, represent a number from 0 to 15. Output P should be TRUE if the number is prime (Hint: A number is prime if it is divisible only by itself and 1; 1 is considered to be prime, and 0 is not). Output D should be TRUE if the number is divisible by 3.

School of Engineering  
BEng (Hons) Electrical and Electronic Engineering  
Semester Two Examination 2018/2019  
Introductory Digital Electronics  
Module No. EEE4013

- (i) Give simplified Boolean equations and Truth Table for each of the outputs P and D. **[12 marks]**
- (ii) Construct the circuit that takes these 4 inputs (A3:0) and produces the output P. **[4 marks]**
- d) Consider a 4-input Boolean function that outputs a binary 1 whenever an odd number of its inputs are binary 1. Using Boolean logic or otherwise, show how the above function can be implemented using only 2-input XOR gates. **[5 marks]**

**Total 25 marks**

**END OF QUESTIONS**

PAST EXAMINATION PAPER