

**UNIVERSITY OF BOLTON**

**SCHOOL OF ENGINEERING**

**B.ENG (HONS) ELECTRICAL & ELECTRONICS  
ENGINEERING**

**EXAMINATION SEMESTER 2 - 2018/2019**

**INTRODUCTORY ANALGQUE ELECTRONICS**

**MODULE NO: EEE4014**

**Date: Wednesday 22<sup>nd</sup> May 2019**

**Time: 10:00am – 12:00pm**

---

**INSTRUCTIONS TO CANDIDATES:**

There are SIX questions.

Answer ANY FOUR questions.

All questions carry equal marks.

Marks for parts of questions are shown in brackets.

Electronic calculators may be used provided that data and program storage memory is cleared prior to the examination.

**CANDIDATES REQUIRE:**

Formula Sheet (attached).

---

UNIVERSITY OF BOLTON  
SCHOOL OF ENGINEERING  
B.ENG (HONS) ELECTRICAL AND ELECTRONIC ENGINEERING  
EXAMINATION SEMESTER 2 - 2018/2019  
INTRODUCTORY ANALGOUE ELECTRONICS  
MODULE NO. EEE4014

Q1

(a)

What is the graphical Volt-ampere characteristic plot of the normal silicon diode and ideal- diode model?

(10 marks)

(b)

Use the ideal-diode model to analyse the circuit as shown in Fig.1(b) to decide the working status of diode D1 and D2. (Please analyse all possible situations with **proper equivalent circuit** for both two diodes).

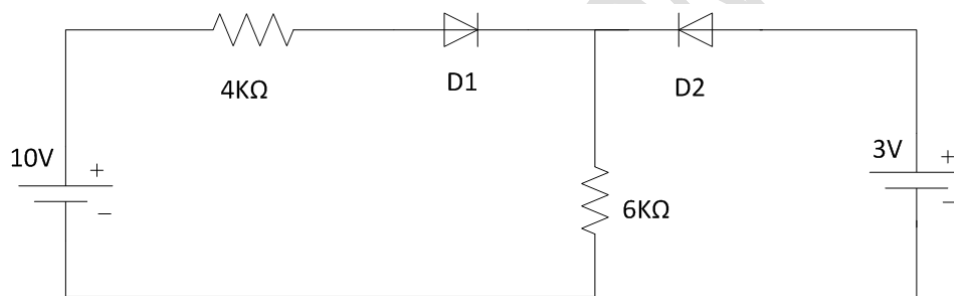


Fig.1(b) Diode circuit model

(15 marks)

Total 25 marks


PLEASE TURN THE PAGE.....

UNIVERSITY OF BOLTON  
 SCHOOL OF ENGINEERING  
 B.ENG (HONS) ELECTRICAL AND ELECTRONIC ENGINEERING  
 EXAMINATION SEMESTER 2 - 2018/2019  
 INTRODUCTORY ANALGOUE ELECTRONICS  
 MODULE NO. EEE4014

Q2.


Using diode or Zener Diode to Design clipper circuits that have the transfer characteristics shown below if 0.6 V drop in the forward direction of diode is set.

(a)

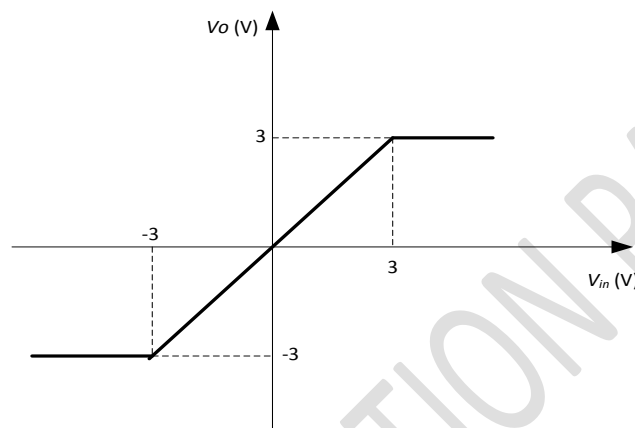

(10 marks)

(b)

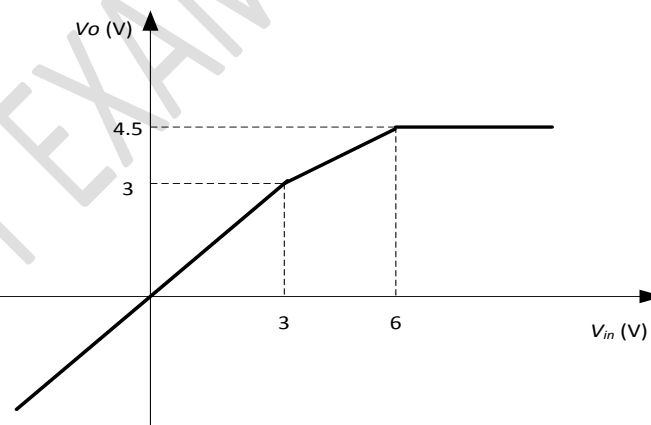

(15 marks)

Total 25 marks

PLEASE TURN THE PAGE.....

UNIVERSITY OF BOLTON  
 SCHOOL OF ENGINEERING  
 B.ENG (HONS) ELECTRICAL AND ELECTRONIC ENGINEERING  
 EXAMINATION SEMESTER 2 - 2018/2019  
 INTRODUCTORY ANALOGUE ELECTRONICS  
 MODULE NO. EEE4014

Q3.

(a) A certain **noninverting** amplifier has a voltage-gain magnitude of 100. The input voltage is  $V_i(t) = 0.5\sin(2000\pi t)$ . What is the expression for output voltage  $V_o(t)$  ?

(5 marks)

(b) If the amplifier is an **inverting** amplifier, repeat the question to find the expression of output voltage  $V_o(t)$ .


(4 marks)

(c) A source with an internal voltage of  $V_s = 1$  mV and an internal resistance of  $R_s = 1$  M $\Omega$  is connected to the input terminals of an amplifier having an open-circuit voltage gain of  $A_{voc} = 10^4$ , an input resistance of  $R_i = 2$  M $\Omega$ , and an output resistance of  $R_o = 2$   $\Omega$ , the load resistance  $R_L = 8$   $\Omega$ .

Find i) Voltage gain  $A_{vs} = V_o/V_s$  and  $A_v = V_o/V_i$ .

ii) Current gain. Note:  $A_i = A_v R_i / R_L$ .

iii) Power gain. Note:  $G = A_v A_i$

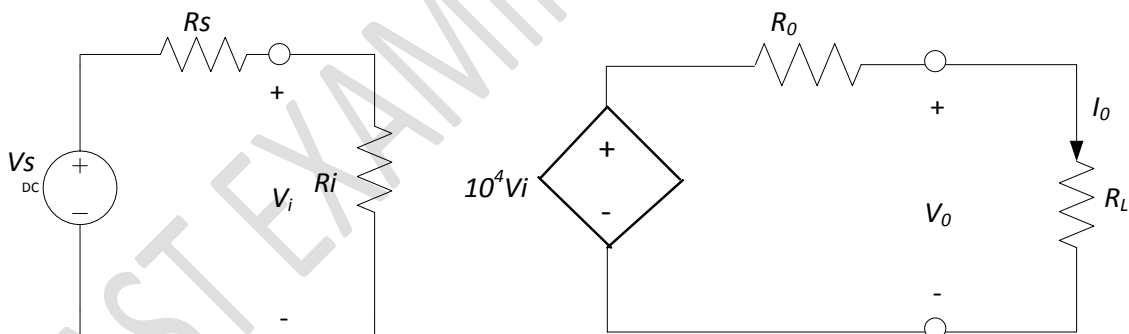

(16 marks)

Total 25 marks


PLEASE TURN THE PAGE.....

UNIVERSITY OF BOLTON  
 SCHOOL OF ENGINEERING  
 B.ENG (HONS) ELECTRICAL AND ELECTRONIC ENGINEERING  
 EXAMINATION SEMESTER 2 - 2018/2019  
 INTRODUCTORY ANALGOUE ELECTRONICS  
 MODULE NO. EEE4014

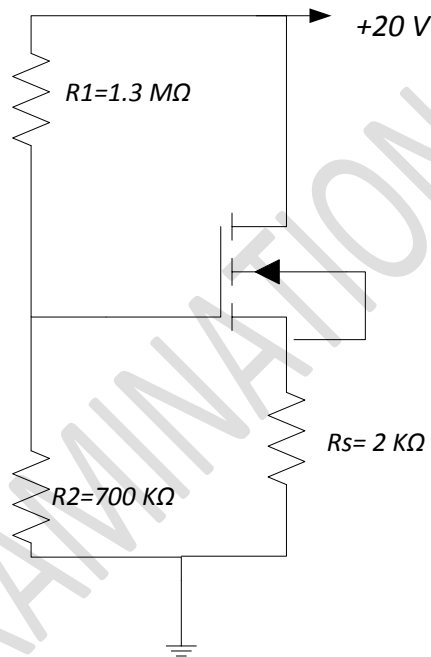Q4.

Analyse the fixed-plus self-bias circuit shown below and determine  $I_{DQ}$  and  $V_{DSQ}$  for the circuit. The FET transistor has  $KP= 50 \mu A/V^2$ ,  $V_{to}=1 V$ ,  $L= 10 \mu m$  and  $W=200 \mu m$ . Please draw the Thevenin equivalent circuit to help the solution.

$$\text{Note: } K = \frac{w KP}{L^2}; I_D = K(V_{GS} - V_{to})^2$$



(25 marks)

Total 25 marks

PLEASE TURN THE PAGE.....

UNIVERSITY OF BOLTON  
SCHOOL OF ENGINEERING  
B.ENG (HONS) ELECTRICAL AND ELECTRONIC ENGINEERING  
EXAMINATION SEMESTER 2 - 2018/2019  
INTRODUCTORY ANALGOUE ELECTRONICS  
MODULE NO. EEE4014

Q5.

Analyse the Four-Resistor Bias BJT transistor Circuit as shown in Fig.Q5.

(a) Determine the value of  $I_C$  and  $V_{CE}$  for the circuit for  $\beta=100$  and  $\beta=300$ .

(16 marks)

(b) Draw the corresponding Thevenin Equivalent Circuit and the equivalent Large-Signal DC circuit model.

(9 marks)

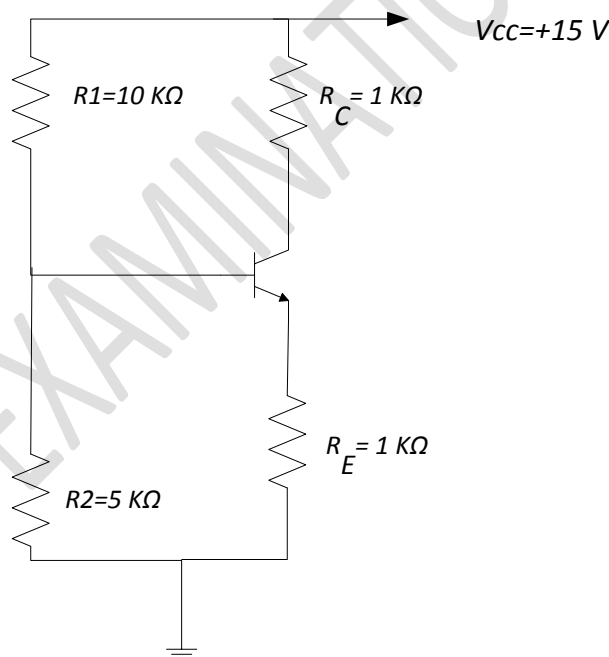


Fig. Q5: A BJT Transistor Circuit

Total 25 marks

PLEASE TURN THE PAGE.....

UNIVERSITY OF BOLTON  
SCHOOL OF ENGINEERING  
B.ENG (HONS) ELECTRICAL AND ELECTRONIC ENGINEERING  
EXAMINATION SEMESTER 2 - 2018/2019  
INTRODUCTORY ANALGOUE ELECTRONICS  
MODULE NO. EEE4014

Q6.

a) An operational amplifier has high input impedance and low output impedance. Briefly explain why this is desirable.

(6 marks)

b) Fig.6b is a diagram of a summing inverting negative feedback operational amplifier circuit with two inputs V1 and V2 and an output Vo. What is the value of Vo if V1=1.5V and V2 = 2.5V ?

(4 marks)

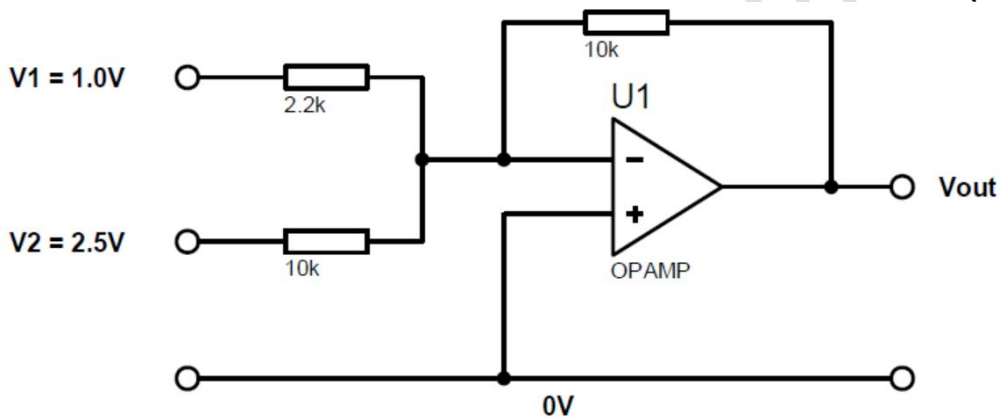


Fig.6b: Summing amplifier (has a supply of +/- 12 V)

Q6 continues over the page...

PLEASE TURN THE PAGE.....

UNIVERSITY OF BOLTON  
 SCHOOL OF ENGINEERING  
 B.ENG (HONS) ELECTRICAL AND ELECTRONIC ENGINEERING  
 EXAMINATION SEMESTER 2 - 2018/2019  
 INTRODUCTORY ANALOGUE ELECTRONICS  
 MODULE NO. EEE4014

**Q6 continued...**

c) Determine the input voltage ( $V_{in1}$ ) from a cascaded operational amplifier circuit as shown in Fig.Q6c.

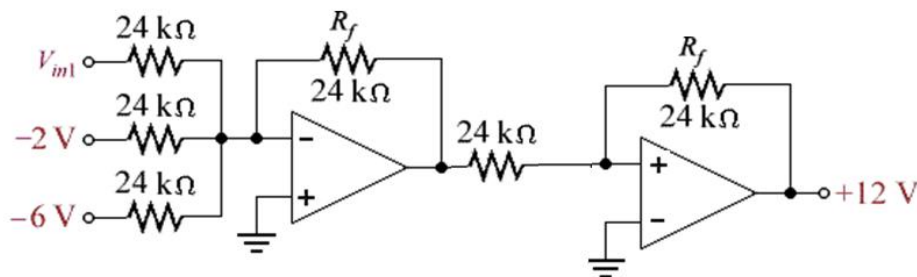


Fig.Q6c: A cascaded operational amplifier circuit.

(7 marks)

d) Briefly define the term common mode rejection ratio. An amplifier has a CMRR of 75 dB. Restate this CMRR as an arithmetic ratio e.g.  $x:1$ , where  $x$  is a numerical value.

(8 marks)

**Total 25 marks**

**END OF QUESTIONS**

**PLEASE TURN THE PAGE FOR FORMULA SHEETS**



UNIVERSITY OF BOLTON  
 SCHOOL OF ENGINEERING  
 B.ENG (HONS) ELECTRICAL AND ELECTRONIC ENGINEERING  
 EXAMINATION SEMESTER 2 - 2018/2019  
 INTRODUCTORY ANALGOUE ELECTRONICS  
 MODULE NO. EEE4014

### Formula sheet

These equations are given to save short-term memorisation of details of derived equations and are given without any explanation or definition of symbols; the student is expected to know the meanings and usage.

Ohms law:  $V=RI$

Power :  $P= IV$

Voltage divider:  $V_{Ri}=V_s(R_i/(R_i+R_s))$

Current gain:  $A_i=I_o/I_i$

Power gain:  $A_P=P_o/P_i=V_oI_o/V_iI_i = A_vA_i$

Bipolar Transistor:

$$I_E=I_B+I_C= (\beta+1) I_B$$

$$I_C=\beta I_B$$

$$r_\pi = V_T/I_B , \text{ where } V_T=0.026V$$

$$I_E = (\beta + 1)I_B$$

$$I_B = \frac{V_B - V_{BE}}{R_B + (\beta + 1)R_E}$$

PLEASE TURN THE PAGE.....

UNIVERSITY OF BOLTON  
 SCHOOL OF ENGINEERING  
 B.ENG (HONS) ELECTRICAL AND ELECTRONIC ENGINEERING  
 EXAMINATION SEMESTER 2 - 2018/2019  
 INTRODUCTORY ANALGOUÉ ELECTRONICS  
 MODULE NO. EEE4014

MOSFET:

$$V_G = (R_2 / (R_1 + R_2)) * V_D$$

$$V_G = V_{GS} + R_s I_D$$

$$I_D = K(V_{GS} - V_t)^2$$

$$V_{DS} = V_{DD} - (R_D + R_s) * I_D$$

$$K = \frac{w KP}{L^2}; I_D = K(V_{GS} - V_{to})^2$$

Operational Amplifier:

$$\frac{V_o}{V_i} = 1 + \frac{R_f}{R_a} \quad \text{----- Non-inverting}$$

$$V_o = -R_f \left( \frac{V_a}{R_a} + \frac{V_b}{R_b} + \frac{V_c}{R_c} \right) = -R_f \sum_{j=a}^c \frac{V_j}{R_j} \quad \text{----- Multiple Inputs}$$

$$\frac{V_o}{V_{in}} = \frac{-R_f}{R_a} \quad \text{----- Inverting}$$

Diode:

$$V_r = \frac{V_M}{2fRC}$$

$$\text{Duty cycle} = \left( \frac{\theta_2 - \theta_1}{2\pi} \right)$$

**END OF FORMULA SHEET**

**END OF PAPER**