

**UNIVERSITY OF BOLTON**  
**SCHOOL OF ENGINEERING**  
**BENG(HONS) ELECTRICAL AND ELECTRONICS**  
**ENGINEERING**  
**SEMESTER 1 EXAMINATION 2023/24**  
**INTRODUCTORY ELECTRICAL PRINCIPLES**  
**MODULE NO: EEE4012**

Date:

Time:

---

**INSTRUCTIONS TO CANDIDATES:**

There are FIVE questions.

Answer ANY FOUR questions.

All questions carry equal marks.

Individual marks are shown within the question.

A formula sheet is given at the end of the paper.

---

School of Engineering  
BEng (Hons) Electrical and Electronics Engineering  
Semester 1 Examination 2023/24  
Introductory Electrical Principles  
Module No. EEE4012

**Question 1**

a) Define the following terms (**1.5 marks for each definition**):

- i. Frequency
- ii. Period
- iii. Phase angle
- iv. Peak to peak value
- v. RMS value
- vi. Internal resistance
- vii. Inductance
- viii. capacitance

**[12 marks]**

b) An AC ammeter reads 22 A rms current through a resistive load, and a voltmeter reads 385 V rms drop across the load.

(i) What are the peak values and the average values of the alternating current and voltage? **[6 marks]**

(ii) Calculate the load resistance. **[2 marks]**

c) Find the Thevenin equivalent of the circuit given in Figure Q1 below. **[5 marks]**

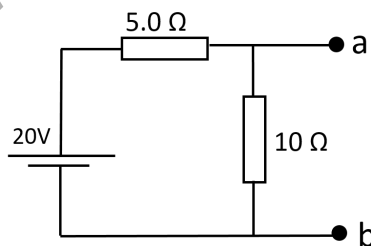


Fig.Q1c

**Total Marks: 25**  
**PLEASE TURN THE PAGE**

### Question 2

- a) A coil of copper wire has a resistance of  $150\ \Omega$ , when its temperature is  $0\ ^\circ\text{C}$ . Determine its resistance at  $60\ ^\circ\text{C}$  if the temperature coefficient of resistance (TCR) of copper at  $0\ ^\circ\text{C}$  is  $0.0043/\ ^\circ\text{C}$ .

[3 marks]

- b) For the following circuit (Figure Q2b), using superposition theorem or otherwise, find out the current flowing through the  $20\ \Omega$  resistor.

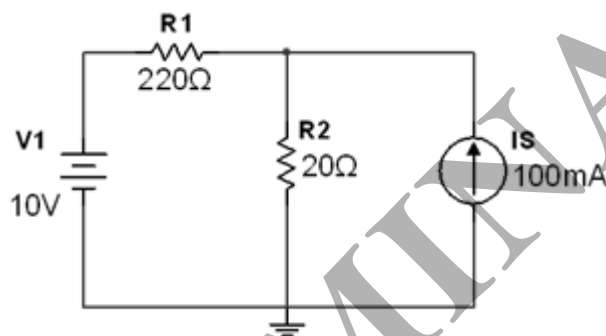


Figure Q2b

[10 marks]

- c) For the circuit shown in Figure Q2c below, calculate:

- (i) the voltage drop across the  $4\ \text{k}\Omega$  resistor [3 marks]  
 (ii) the current through the  $5\ \text{k}\Omega$  resistor [3 marks]  
 (iii) the power developed in the  $1.5\ \text{k}\Omega$  resistor [3 marks]  
 (iv) the voltage at point X w.r.t. earth [3 marks]

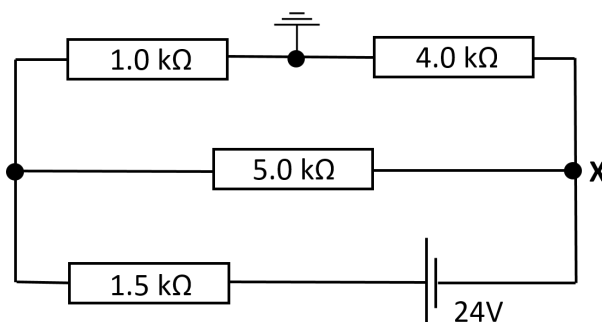


Figure Q2c

Total Marks: 25

PLEASE TURN THE PAGE

### Question 3

- a) A  $4.7 \mu\text{F}$  capacitor has 12 V across it. What quantity of charge is stored in it? **[3 marks]**
- b) Draw a diagram of a parallel plate capacitor, showing the charge on the plates and the **E** field in the region between the plates. **[5 marks]**
- c) Explain what is meant by the dielectric strength **E<sub>m</sub>** of an insulator? **[4 marks]**
- d) For the capacitor **charging** circuit shown in figure Q3d below, where the capacitor is initially discharged, sketch two separate graphs for the current *I* versus time and the capacitor voltage *V<sub>c</sub>* versus time. **[8 marks]**

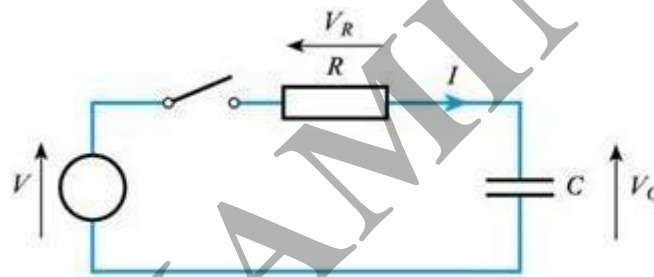


Figure Q3d An initially uncharged capacitor being charged through a resistor.

- e) Explain with the assistance of a diagram what happens to the structure of the curves for *I* versus time and *V<sub>c</sub>* versus time if the time constant  $\tau = RC$  for the circuit increases? **[5 marks]**

**Total Marks: 25**

### Question 4

For the circuit shown in figure Q4 , calculate:

- |                                                           |           |
|-----------------------------------------------------------|-----------|
| a) Currents $I_1$ , $I_2$ , and $I_3$                     | [9 marks] |
| b) Voltages across $R_1$ , $R_2$ , and $R_3$              | [6 marks] |
| c) Powers $P_1$ , $P_2$ , and $P_3$                       | [3 marks] |
| d) Draw the complete voltages and currents phasor diagram | [3 marks] |
| e) The peak $I_3$ current at resonance frequency          | [4 marks] |

Where  $v = 17\cos 314t$  ,  $R_1 = R_2 = 2\Omega$  ,  $R_3 = 4\Omega$  ,  $X_{L2} = j2\Omega$  ,  $X_{L3} = j6\Omega$  ,  $X_C = -j4\Omega$

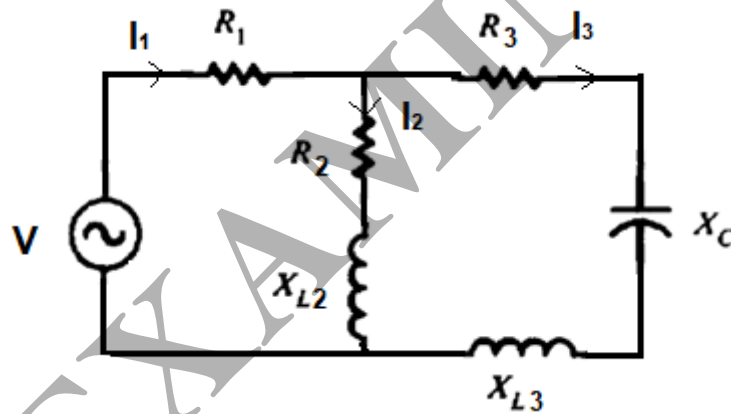


Figure Q4

Total Marks: 25

PLEASE TURN THE PAGE

School of Engineering  
 BEng (Hons) Electrical and Electronics Engineering  
 Semester 1 Examination 2023/24  
 Introductory Electrical Principles  
 Module No. EEE4012

**Question 5**

- a) Explain why AC current through an inductor lags AC voltage across the inductor by 90 degrees, give the physical and mathematical interpretation for this phase difference.

**[6 marks]**

- b) For a single-phase transformer of rated power of 250 V.A, what would be its secondary voltage and current if it has turns ratio ( $\frac{N_1}{N_2}$ ) of 10:1(step down) when it is connected to a supply mains of 250 V, 50 Hz.

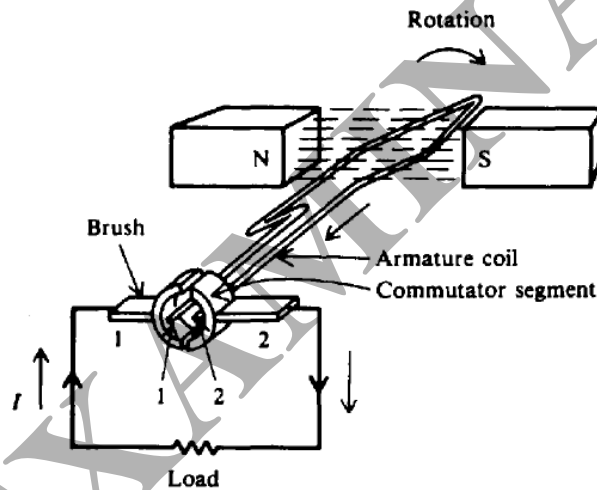
**[5 marks]**

Fig.Q5c

- c) If the DC generator shown above in Fig.Q5c generates 8 volts (peak value) across the brushes, what would be the rms current that flows in the 1-  $\Omega$  load? **[3 marks]**
- d) An AC motor is running at 1500 revolutions per minute when supplied from a 50 Hz supply mains, what would be its number of magnetic poles? **[4 marks]**
- e) Design the clock signal frequency of a steps motor to rotate at 300 rpm +/- 10 rpm. Given that the stepper motor has the accuracy of 2.5 degree per step

**[7 marks]****Total Marks: 25****END OF QUESTIONS PLEASE TURN PAGE FOR FORMULA SHEET**

School of Engineering  
 BEng (Hons) Electrical and Electronics Engineering  
 Semester 1 Examination 2023/24  
 Introductory Electrical Principles  
 Module No. EEE4012

### APPENDIX: Formula Sheet

The following symbols in the formulae have their standard meaning:

Ohm's law:  $V = IR$

Power:  $P = IV$

Magnetic flux:  $\Phi = BA$

Induced voltage:  $V = \Delta\Phi/\Delta t$

$$f = \frac{pn}{120}$$

Magnitude of the Reactance of Inductor  $L$ :  $X_L = 2\pi fL$

Magnitude of the Reactance of Capacitor  $C$ :  $X_C = \frac{1}{2\pi fC}$

Pythagorean theorem:  $c^2 = a^2 + b^2$

Tangent function:  $\tan A = \text{opposite}/\text{adjacent}$

Multiply the Value	By	To Get the Value
Peak	2	Peak-to-peak
Peak-to-peak	0.5	Peak
Peak	0.637	Average
Average	1.570	Peak
Peak	0.707	RMS (effective)
RMS (effective)	1.414	Peak
Average	1.110	RMS (effective)
RMS (effective)	0.901	Average

PLEASE TURN THE PAGE


**Summary Table for Series and Parallel RC Circuits**

$X_C$ and $R$ in Series	$X_C$ and $R$ in Parallel
$I$ the same in $X_C$ and $R$	$V_T$ the same across $X_C$ and $R$
$V_T = \sqrt{V_R^2 + V_C^2}$	$I_T = \sqrt{I_R^2 + I_C^2}$
$Z = \sqrt{R^2 + X_C^2} = \frac{V_T}{I}$	$Z_T = \frac{V_T}{I_T}$
$V_C$ lags $V_R$ by $90^\circ$	$I_C$ leads $I_R$ by $90^\circ$
$\theta = \arctan\left(-\frac{X_C}{R}\right)$	$\theta = \arctan\frac{I_C}{I_R}$

**Summary Table for Series and Parallel RL Circuits**

$X_L$ and $R$ in Series	$X_L$ and $R$ in Parallel
$I$ the same in $X_L$ and $R$	$V_T$ the same across $X_L$ and $R$
$V_T = \sqrt{V_R^2 + V_L^2}$	$I_T = \sqrt{I_R^2 + I_L^2}$
$Z = \sqrt{R^2 + X_L^2} = \frac{V_T}{I}$	$Z_T = \frac{V_T}{I_T}$
$V_R$ lags $V_L$ by $90^\circ$	$I_L$ lags $I_R$ by $90^\circ$
$\theta = \arctan\frac{X_L}{R}$	$\theta = \arctan\left(-\frac{I_L}{I_R}\right)$

Three-phase systems:

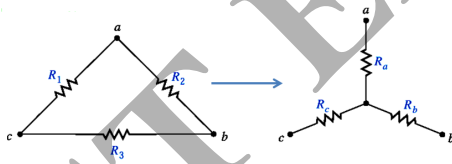


$$R_a = \frac{R_1 R_2}{R_1 + R_2 + R_3}$$

$$R_b = \frac{R_2 R_3}{R_1 + R_2 + R_3}$$

$$R_c = \frac{R_3 R_1}{R_1 + R_2 + R_3}$$

Delta to Star conversion:

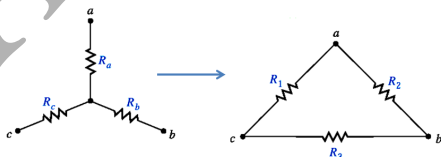

$$R_1 = \frac{R_a R_b + R_b R_c + R_c R_a}{R_b}$$

$$R_2 = \frac{R_a R_b + R_b R_c + R_c R_a}{R_c}$$

$$R_3 = \frac{R_a R_b + R_b R_c + R_c R_a}{R_a}$$

Star to Delta conversion:

**END OF PAPER**