

**UNIVERSITY OF BOLTON**  
**SCHOOL OF ENGINEERING**  
**BENG(HONS) ELECTRICAL AND ELECTRONICS**  
**ENGINEERING**  
**SEMESTER 1 EXAM 2024/25**  
**INTRODUCTORY ELECTRICAL PRINCIPLES**  
**MODULE NO: EEE4012**

Date: Monday 13<sup>th</sup> January 2025

Time: 2:00pm – 4:00pm

---

**INSTRUCTIONS TO CANDIDATES:**

There are FIVE questions.

Answer ANY FOUR questions.

All questions carry equal marks.

Individual marks are shown within the question.

A formula sheet is given at the end of the paper.

---

### Question 1

a) Define the following terms (**1.5 marks for each definition**):

- i. Frequency
- ii. Period
- iii. Phase angle
- iv. Peak to peak value
- v. RMS value
- vi. Internal resistance

**[9 marks]**

b) An AC ammeter reads 11A rms current through a resistive load, and a voltmeter reads 360V rms drop across the load.

(i) What are the peak values and the average values of the alternating current and voltage? **[6 marks]**

(ii) Calculate the load resistance. **[2 marks]**

c) Find the  $V_{AG}$  and  $V_{BG}$  in the circuit given in Figure Q1c below. **[8 marks]**

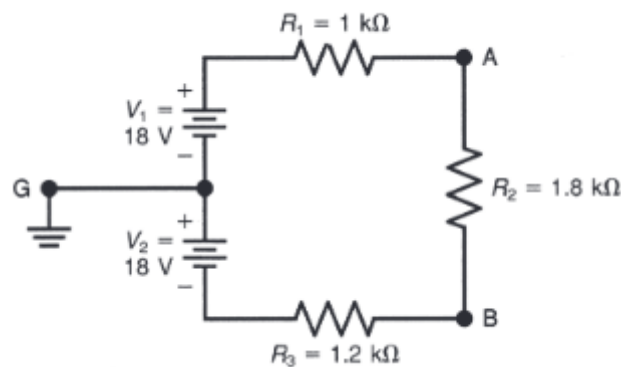


Fig.Q1c

**Total Marks: 25**  
**PLEASE TURN THE PAGE**

**Question 2**

- a) A coil of aluminium wire has a resistance of  $50\ \Omega$ , when its temperature is  $0\ ^\circ\text{C}$ . Determine its resistance at  $100\ ^\circ\text{C}$  if the temperature coefficient of resistance (TCR) of aluminium at  $0\ ^\circ\text{C}$  is  $0.0038/^\circ\text{C}$ .

**[3 marks]**

- b) For the following circuit (Figure Q2b), using superposition theorem or otherwise, find out the current flowing through the  $10\ \Omega$  resistor.

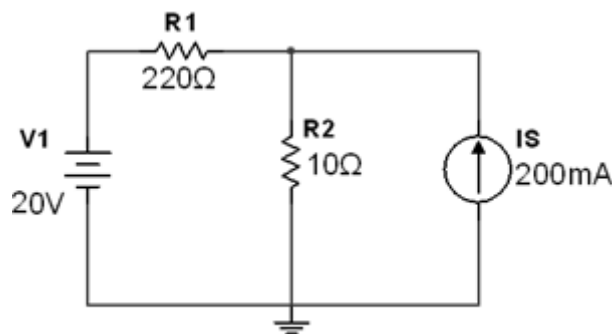
**[10 marks]**

Figure Q2b

- c) For the circuit shown in figure Q2c below, calculate:

- |   |                  |
|---|------------------|
| (i) the voltage drop across the $4\ \text{k}\Omega$ resistor    | <b>[3 marks]</b> |
| (ii) the current through the $5\ \text{k}\Omega$ resistor       | <b>[3 marks]</b> |
| (iii) the power developed in the $1.5\ \text{k}\Omega$ resistor | <b>[3 marks]</b> |
| (iv) the voltage at point X w.r.t. earth                        | <b>[3 marks]</b> |

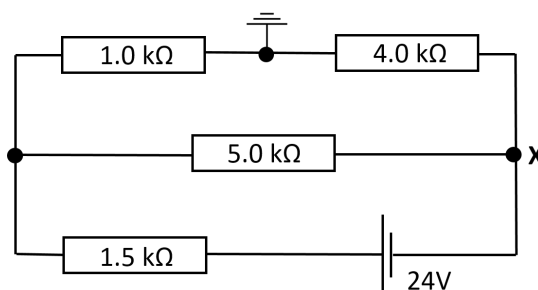


Fig.Q2c

**Total Marks: 25**  
**PLEASE TURN THE PAGE**

### Question 3

- a) In the circuit given in figure Q3a below, use appropriate network conversion ( $\Delta$  to Y/Y to  $\Delta$ ) to find the total current supplied by  $V_T$ . **[15 marks]**

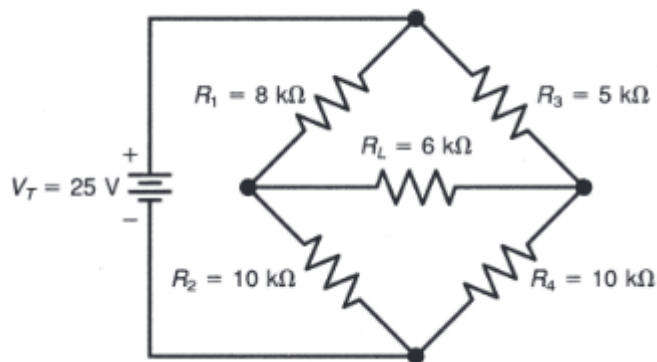


Fig.Q3a

- b) Use Thevenins Theorem to calculate the voltage and current through the resistor  $R_L$ . **[10 marks]**

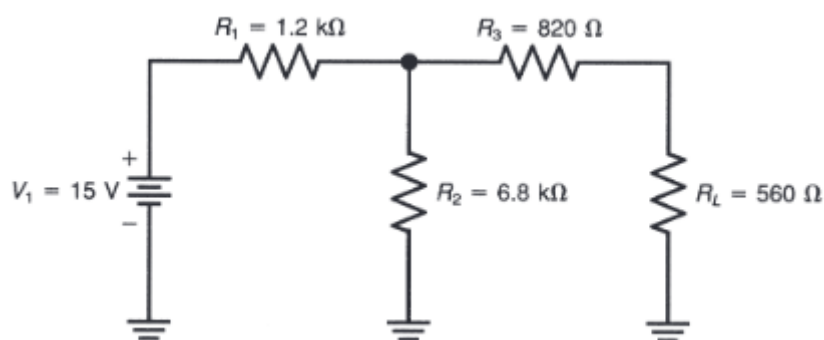


Fig.Q3b

**Total Marks: 25**  
**PLEASE TURN THE PAGE**

#### Question 4

a) For the circuit shown in Fig. Q4,  $R=30\Omega$ ,  $L=150\text{mH}$  and  $C=100\mu\text{F}$  calculate:

- The inductive reactance and the capacitive reactance; [2 marks]
- The current through each branch,  $I_R$ ,  $I_L$  and  $I_C$ ; [3 marks]
- The total current  $I_T$ ; [3 marks]
- The phase angle between the voltage and the total current  $\theta$ ; [3 marks]
- The total impedance  $Z$ ; [3 marks]
- Is the circuit inductive or capacitive and why? [3 marks]
- The resonance frequency. [3 marks]

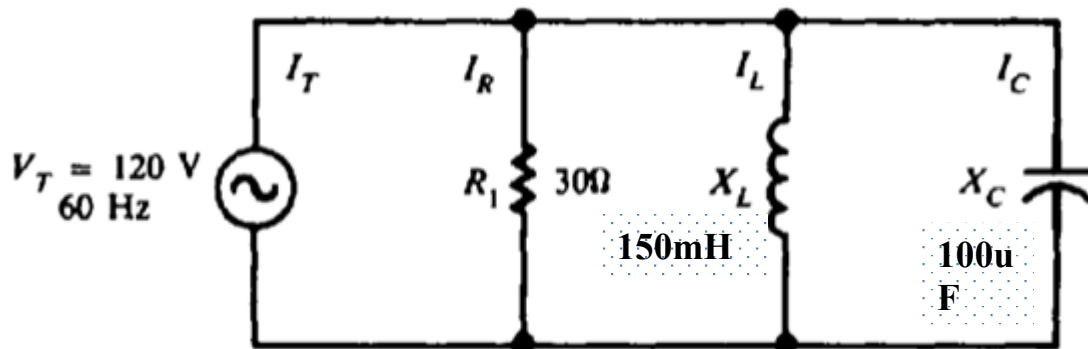


Figure Q4

b) For a single-phase transformer of rated power of 250 V.A, what would be its secondary voltage and current if it has turns ratio ( $N_1/N_2$ ) of 10:1(step down) when it is connected to a supply mains of 250 V, 50 Hz. [5 marks]

**Total Marks: 25**  
**PLEASE TURN THE PAGE**

**Question 5**

a) What is the inductance of an inductor if the number of turns is 100 turns, relative permeability of 1000, and coil area to coil length ratio is 3? **[3 marks]**

b) In a resistance-capacitor circuit shown in Figure Q5.b, the voltage drop across points A and B is 28.28 V. If the frequency of the current is 1 kHz,

(i) Find the voltage across the resistor. **[6 marks]**

(ii) Draw the phasor diagram. **[4 marks]**

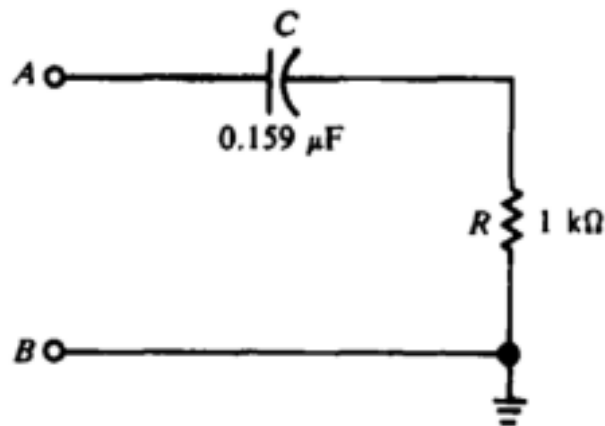


Figure Q5b

c) An 8-pole AC motor is running at a synchronous speed of 750 revolution per minute, what would be supply frequency? **[2 marks]**

d) A stepper motor has an angular resolution of 9 degrees per step. Find out the motor speed in rpm if the frequency is 50 Hz. **[10 marks]**

**Total Marks: 25**

**END OF QUESTIONS**

**PLEASE TURN THE PAGE FOR FORMULA SHEET**

School of Engineering  
 BEng (Hons) Electrical and Electronics Engineering  
 Semester 1 Examination 2024/25  
 Introductory Electrical Principles  
 Module No. EEE4012

### APPENDIX: Formula Sheet

The following symbols in the formulae have their standard meaning:

$$R\theta = R0(1 + \alpha \cdot \theta)$$

Ohm's law:  $V = IR$

Power:  $P = IV$

Magnetic flux:  $\Phi = BA$

Induced voltage:  $V = \Delta\Phi/\Delta t$

$$f = \frac{pn}{120}$$

Magnitude of the Reactance of Inductor  $L$ :  $X_L = 2\pi fL$

Magnitude of the Reactance of Capacitor  $C$ :  $X_C = \frac{1}{2\pi fC}$

Pythagorean theorem:  $c^2 = a^2 + b^2$

Tangent function:  $\tan A = \text{opposite/adjacent}$

Multiply the Value	By	To Get the Value
Peak	2	Peak-to-peak
Peak-to-peak	0.5	Peak
Peak	0.637	Average
Average	1.570	Peak
Peak	0.707	RMS (effective)
RMS (effective)	1.414	Peak
Average	1.110	RMS (effective)
RMS (effective)	0.901	Average

**PLEASE TURN THE PAGE**


**Summary Table for Series and Parallel RC Circuits**

$X_C$ and $R$ in Series	$X_C$ and $R$ in Parallel
$I$ the same in $X_C$ and $R$	$V_T$ the same across $X_C$ and $R$
$V_T = \sqrt{V_R^2 + V_C^2}$	$I_T = \sqrt{I_R^2 + I_C^2}$
$Z = \sqrt{R^2 + X_C^2} = \frac{V_T}{I}$	$Z_T = \frac{V_T}{I_T}$
$V_C$ lags $V_R$ by $90^\circ$	$I_C$ leads $I_R$ by $90^\circ$
$\theta = \arctan\left(-\frac{X_C}{R}\right)$	$\theta = \arctan \frac{I_C}{I_R}$

**Summary Table for Series and Parallel RL Circuits**

$X_L$ and $R$ in Series	$X_L$ and $R$ in Parallel
$I$ the same in $X_L$ and $R$	$V_T$ the same across $X_L$ and $R$
$V_T = \sqrt{V_R^2 + V_L^2}$	$I_T = \sqrt{I_R^2 + I_L^2}$
$Z = \sqrt{R^2 + X_L^2} = \frac{V_T}{I}$	$Z_T = \frac{V_T}{I_T}$
$V_R$ lags $V_L$ by $90^\circ$	$I_L$ lags $I_R$ by $90^\circ$
$\theta = \arctan \frac{X_L}{R}$	$\theta = \arctan\left(-\frac{I_L}{I_R}\right)$

Three-phase systems:

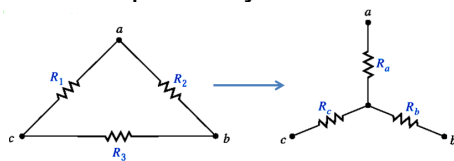


$$R_a = \frac{R_1 R_2}{R_1 + R_2 + R_3}$$

$$R_b = \frac{R_2 R_3}{R_1 + R_2 + R_3}$$

$$R_c = \frac{R_3 R_1}{R_1 + R_2 + R_3}$$

Delta to Star conversion:

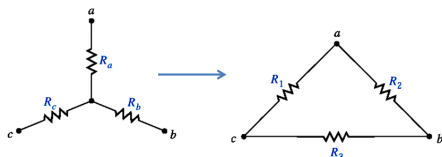

$$R_1 = \frac{R_a R_b + R_b R_c + R_c R_a}{R_b}$$

$$R_2 = \frac{R_a R_b + R_b R_c + R_c R_a}{R_c}$$

$$R_3 = \frac{R_a R_b + R_b R_c + R_c R_a}{R_a}$$

Star to Delta conversion:

**END OF PAPER**