

UNIVERSITY OF BOLTON
SCHOOL OF ENGINEERING
BENG (HONS) ELECTRICAL AND ELECTRONIC
ENGINEERING
EXAMINATION SEMESTER 1 - 2024/2025
INTERMEDIATE ELECTRICAL PRINCIPLES &
ENABLING POWER ELECTRONICS
MODULE NO: EEE5013

Date: Wednesday 8th January 2025

Time: 10:00 – 12:30pm

INSTRUCTIONS TO CANDIDATES:

There are FIVE questions.

Answer ANY FOUR questions.

All questions carry equal marks.

Marks for parts of questions are shown in brackets.

This examination paper carries a total of 100 marks.

All working must be shown. A numerical solution to a question obtained by programming an electronic calculator will not be accepted.

CANDIDATES REQUIRE:

Formula Sheet(attached).

Question 1

- a) An operational amplifier has high input impedance and low output impedance. Briefly explain why this is desirable.

[6 marks]

- b) Figure Q1b below is a diagram of a summing inverting negative feedback operational amplifier circuit with two inputs V_1 and V_2 and an output V_{out} .

i) Derive an expression for the output V_{out} of the following circuit in terms of the input voltages V_1 and V_2

ii) What is the value of V_{out} if $V_1=2\text{ V}$ and $V_2 = 3\text{ V}$?

[10 marks]

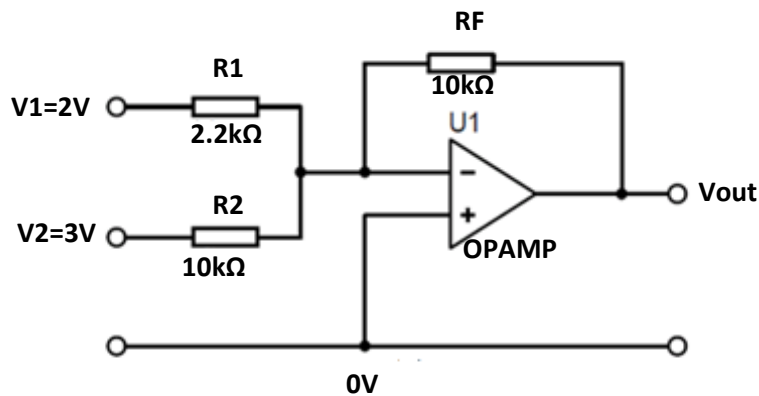


Fig.Q1b: Summing amplifier (has a supply of +/- 12 V)

- c) An instrumentation amplifier is often used to obtain a high signal to noise ratio and it achieves this by common-mode rejection. Briefly define the term common mode rejection ratio.

[5 marks]

- d) An amplifier has a common mode rejection ratio of 86 dB. Express the common mode rejection ratio as an arithmetic ratio e.g. $x:1$, where x is a numerical value.

[4 marks]

Total 25 marks

PLEASE TURN THE PAGE

Question 2

- a) Enumerate the basic grounding system then explain what is meant by static grounding.

[4 marks]

- b) For the following two devices if they carry the same load current of 12 A (rms) find their respective junction temperature (T_J), temperature of the junction region of the following semiconductor devices, at steady state. Assume ambient temperature = 25°C and $R_{\theta ca} = 3^\circ\text{C/W}$. $R_{DS(on)}$ = drain - source on resistance, $P_{D(max)}$ = Maximum power dissipation, $R_{\theta ca}$ = Thermal Resistance between case-ambient and $R_{\theta jc}$ = Thermal Resistance between junction-case.

	<u>Device 1 (IRF531)</u>	<u>Device 2 (MTP14N06A)</u>
1. $R_{DS(on)}$	0.18 Ω	0.10 Ω
2. $R_{\theta jc}$	1.67 $^\circ\text{C/W}$	3.12 $^\circ\text{C/W}$
3. $P_{D(max)}$	75W	40W

[14 marks]

- c) For a dam in an electro hydro power station with the head on a dam is 4500cm.

- I. What is the potential energy for one m^3 of water at the top of the reservoir?

[4 marks]


- II. If this passes a turbine in 1 second, what total power does it represent? Ignore friction.

[3 marks]**Total 25 Marks****PLEASE TURN THE PAGE**

Question 3

a) The single-phase half-wave-controlled rectifier shown in **Figure Q3a** supplies a resistive load with an average load current of 1.62 A. If the supply voltage is 240 V, 50 Hz and the average output voltage is 81 V, calculate the following:

- | | |
|---------------------------------------|------------------|
| I. The firing angle α | [4 marks] |
| II. The load resistor R | [2 marks] |
| III. The rms load voltage | [3 marks] |
| IV. The rms load current | [2 marks] |
| V. The DC power and the ripple factor | [4 marks] |

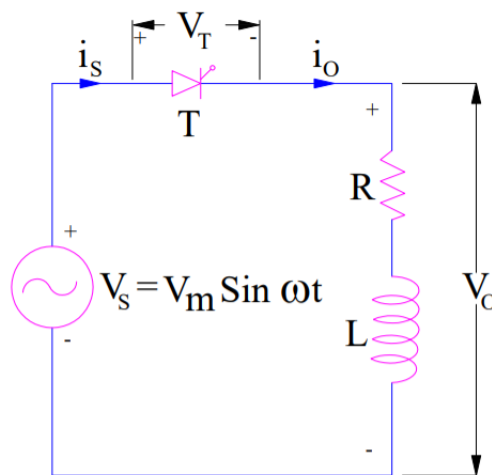**Figure Q3a**

b) The Xlinks Morocco-UK Power project is a proposal that is capable of transmitting up to 3.6 GW solar and wind-generated electricity from Morocco to the United Kingdom. If built, the 4,000 km (2,500 miles) cable will be the world's longest undersea power cable, and would supply up to 8% of the UK's electricity consumption.

Analyse whether an AC or DC transmission system would be more suitable for this project, considering at least 3 out of the 4 following factors:

- Line losses
- Installation and maintenance costs

Question 3 continues over the page....

PLEASE TURN THE PAGE

Question 3 continued....

- Ease of integration with existing grid infrastructure
- Impact on the stability of the power system

[8 marks]

c) What type of DC-DC converter is represented in the circuit diagram shown in Figure Q3c? Choose the correct answer from the four provided options.

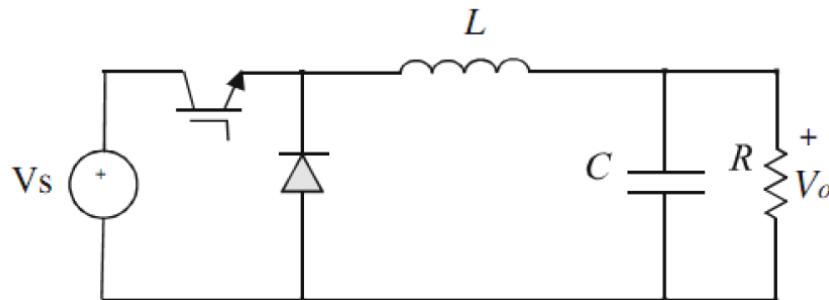


Figure Q3c

- Step-up/Boost converter
- Step-down/Buck converter
- Inverter
- Buck-Boost converter

[2 marks]

Total 25 Marks

PLEASE TURN THE PAGE

Question 4

- (a) Calculate the line voltages and the line currents of a Y-Y source-load Connection.
Given: $V_{an} = 120 \angle 60^\circ \text{ V}$. The system is a positive sequence, balanced three-phase system. The system impedances per phase are given as follows:

$$Z_{\text{source}} = 0.4 + j0.3 \, \Omega, \, Z_{\text{line}} = 0.6 + j0.7 \, \Omega, \text{ and } Z_{\text{load}} = 24 + j19 \, \Omega.$$

[10 Marks]

- (b) Assume a delta-connected load, with each leg $Z = 100 \angle 80^\circ \, \Omega$, is supplied from a Y-connected 3-phase supply with voltage of 13.8 kV (L-L) source. Find:

- (i) The complex power of the source and load.

[6 marks]

- (ii) The power factor at the load.

[4 marks]

- (iii) The value of a shunt capacitor that brings the power factor of the load to unity.
Assume system frequency is 50 Hz

[5 marks]

Total 25 Marks

PLEASE TURN THE PAGE

Question 5

- a) A 3-phase, 50 Hz, 215 kV power line is delivering load of 125 MW at 0.8 power factor lagging and has an impedance per phase of $186.78 \angle 79.46^\circ \Omega$. Find out what is the value of a series capacitance that compensates 70% of its inductive reactance. **[5 marks]**
- b) Draw a circuit diagram for a boost converter using components of inductor, capacitor, switch, load resistor and a diode, and explain its operation in continuous conduction mode (CCM). **[10 marks]**
- c) For the above boost converter, if the input voltage is 20 V, the switch operates at $T_{ON} = 0.36$ msec, $T_{OFF} = 0.14$ msec, calculate the following:
- (i) the chopping frequency and the Duty Cycle **[2 marks]**
 - (ii) The average value of the output voltage **[3 marks]**
 - (iii) The average value of the output current, if the resistance load is 10Ω **[2 marks]**
 - (iv) The changes in inductor current ΔI_L , if the inductance is 10 mH **[3 marks]**

Total 25 Marks

END OF QUESTIONS

PLEASE TURN THE PAGE FOR FORMULA SHEETS

Formula sheet

These equations are given to save short-term memorisation of details of derived equations and are given without any explanation or definition of symbols; the student is expected to know the meanings and usage.

Converters:

$$\begin{aligned}\% \text{THD}_i &= 100 \times \frac{I_{\text{dis}}}{I_{s1}} \\ &= 100 \times \frac{\sqrt{I_s^2 - I_{s1}^2}}{I_{s1}} \\ &= 100 \times \sqrt{\sum_{h \neq 1} \left(\frac{I_{sh}}{I_{s1}} \right)^2}\end{aligned}$$

$$\text{PF} = \frac{V_s I_{s1} \cos \phi_1}{V_s I_s} = \frac{I_{s1}}{I_s} \cos \phi_1$$

$$\text{DPF} = \cos \phi_1$$

$$\text{PF} = \frac{I_{s1}}{I_s} \text{DPF}$$

$$\text{PF} = \frac{1}{\sqrt{1 + \text{THD}_i^2}} \text{DPF}$$

$$A_u = \sqrt{2} V_s (1 - \cos u) = \omega L_s I_d$$

$$\cos u = 1 - \frac{\omega L_s I_d}{\sqrt{2} V_s}$$

$$V_d = 0.45 V_s - \frac{\text{area } A_u}{2\pi} = 0.45 V_s - \frac{\omega L_s}{2\pi} I_d$$

$$V_d = 1.35 V_{LL} \cos \alpha - 3 \frac{\omega L_s}{\pi} I_d$$

$$\cos(\alpha + u) = \cos \alpha - 2 \frac{\omega L_s}{\sqrt{2} V_{LL}} I_d$$

$$\gamma = 180 - (\alpha + u)$$

$$V_L = \left[\frac{1}{T} \int_0^T v_L^2(t) dt \right]^{1/2}$$

$$V_{dc} = \frac{1}{T} \int_0^T v_L(t) dt$$

PLEASE TURN THE PAGE

School of Engineering

BEng (Hons) Electrical and Electronic Engineering

Semester 1 Examination 2024/2025

INTERMEDIATE ELECTRICAL PRINCIPLES & ENABLING POWER ELECTRONICS

Module No. EEE5013

$$\text{TUF} = \frac{P_{dc}}{V_s I_s} = \frac{V_{dc} I_{dc}}{V_s I_s}$$

$$\text{RF} = \frac{V_{ac}}{V_{dc}}$$

$$\sigma = \frac{P_{dc}}{P_L} = \frac{V_{dc} I_{dc}}{V_L I_L}$$

$$\text{FF} = \frac{V_L}{V_{dc}} \quad \text{or} \quad \frac{I_L}{I_{dc}}$$

$$V_{da} = \frac{1}{2\pi} \int_{\alpha}^{\pi} V_{max} \sin(\omega t) d(\omega t) = \frac{V_{max}}{2\pi} (1 + \cos \alpha)$$

$$V_{ph} = \frac{V}{\sqrt{3}}, I_{ph} = I \quad \text{for star connection,}$$

$$V_{ph} = V, I_{ph} = \frac{I}{\sqrt{3}} \quad \text{for delta connection}$$


$$V_{ph} = \frac{V}{\sqrt{3}}, I_{ph} = I \quad \text{for star connection, } V_{ph} = V, I_{ph} = \frac{I}{\sqrt{3}} \quad \text{for delta connection}$$

$$S = \sqrt{3}VI \quad \text{V.A.}, P = \sqrt{3}VI \cos \theta \quad \text{W.}, Q = \sqrt{3}VI \sin \theta \quad \text{V.A.r}$$


$$Q_C = \sqrt{3}VI_C \quad \text{V.A.r}, X_C = \frac{V}{\sqrt{3}I_C} \quad \Omega$$

PLEASE TURN THE PAGE

Three-phase systems

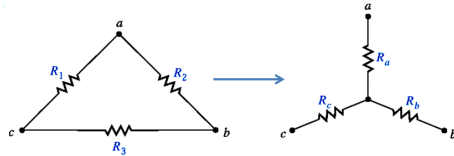

Delta to Star conversion:

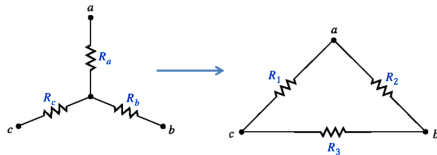

Star to Delta conversion:

Gravity:

Thermal resistance of the interface material:

Output voltage of a differentiator circuit:

Compressibility relationship:

Force on a submerged wall:

$$R_a = \frac{R_1 R_2}{R_1 + R_2 + R_3}$$

$$R_b = \frac{R_2 R_3}{R_1 + R_2 + R_3}$$

$$R_c = \frac{R_3 R_1}{R_1 + R_2 + R_3}$$

$$R_1 = \frac{R_a R_b + R_b R_c + R_c R_a}{R_b}$$

$$R_2 = \frac{R_a R_b + R_b R_c + R_c R_a}{R_c}$$

$$R_3 = \frac{R_a R_b + R_b R_c + R_c R_a}{R_a}$$

$$9.81 \text{ m/s}^2$$

$$\theta_{cs} = \frac{(\rho)(t)}{A}$$

$$v_0 = -R_2 C_1 \frac{dv_I}{dt}$$

$$K = -V \frac{dP}{dV}$$

$$F = \frac{\rho g a h^2}{2}$$

PLEASE TURN THE PAGE

Summary of phase and line voltages/currents for
 balanced three-phase systems.¹

Connection	Phase voltages/currents	Line voltages/currents
Y-Y	$V_{an} = V_p \angle 0^\circ$ $V_{bn} = V_p \angle -120^\circ$ $V_{cn} = V_p \angle +120^\circ$ Same as line currents	$V_{ab} = \sqrt{3}V_p \angle 30^\circ$ $V_{bc} = V_{ab} \angle -120^\circ$ $V_{ca} = V_{ab} \angle +120^\circ$ $I_a = V_{an}/Z_Y$ $I_b = I_a \angle -120^\circ$ $I_c = I_a \angle +120^\circ$
Y-Δ	$V_{an} = V_p \angle 0^\circ$ $V_{bn} = V_p \angle -120^\circ$ $V_{cn} = V_p \angle +120^\circ$ $I_{AB} = V_{AB}/Z_\Delta$ $I_{BC} = V_{BC}/Z_\Delta$ $I_{CA} = V_{CA}/Z_\Delta$	$V_{ab} = V_{AB} = \sqrt{3}V_p \angle 30^\circ$ $V_{bc} = V_{BC} = V_{ab} \angle -120^\circ$ $V_{ca} = V_{CA} = V_{ab} \angle +120^\circ$ $I_a = I_{AB} \sqrt{3} \angle -30^\circ$ $I_b = I_a \angle -120^\circ$ $I_c = I_a \angle +120^\circ$
Δ-Δ	$V_{ab} = V_p \angle 0^\circ$ $V_{bc} = V_p \angle -120^\circ$ $V_{ca} = V_p \angle +120^\circ$ $I_{AB} = V_{ab}/Z_\Delta$ $I_{BC} = V_{bc}/Z_\Delta$ $I_{CA} = V_{ca}/Z_\Delta$	Same as phase voltages $I_a = I_{AB} \sqrt{3} \angle -30^\circ$ $I_b = I_a \angle -120^\circ$ $I_c = I_a \angle +120^\circ$
Δ-Y	$V_{ab} = V_p \angle 0^\circ$ $V_{bc} = V_p \angle -120^\circ$ $V_{ca} = V_p \angle +120^\circ$ Same as line currents	Same as phase voltages $I_a = \frac{V_p \angle -30^\circ}{\sqrt{3}Z_Y}$ $I_b = I_a \angle -120^\circ$ $I_c = I_a \angle +120^\circ$

END OF PAPER